

# Current Electricity

- What is Current Electricity?
- Electrical Circuits
- Electrochemical Cells
  - Wet, Dry and Fuel Cells



# Current Electricity

**Current Electricity** – continuous flow of electrons in a closed circuit

A flow of electrons moves continuously as long as there is:

1. An energy source
2. A complete path




# Electrical Circuits

**Circuit** = complete path of electron flow

Parts of a Circuit:

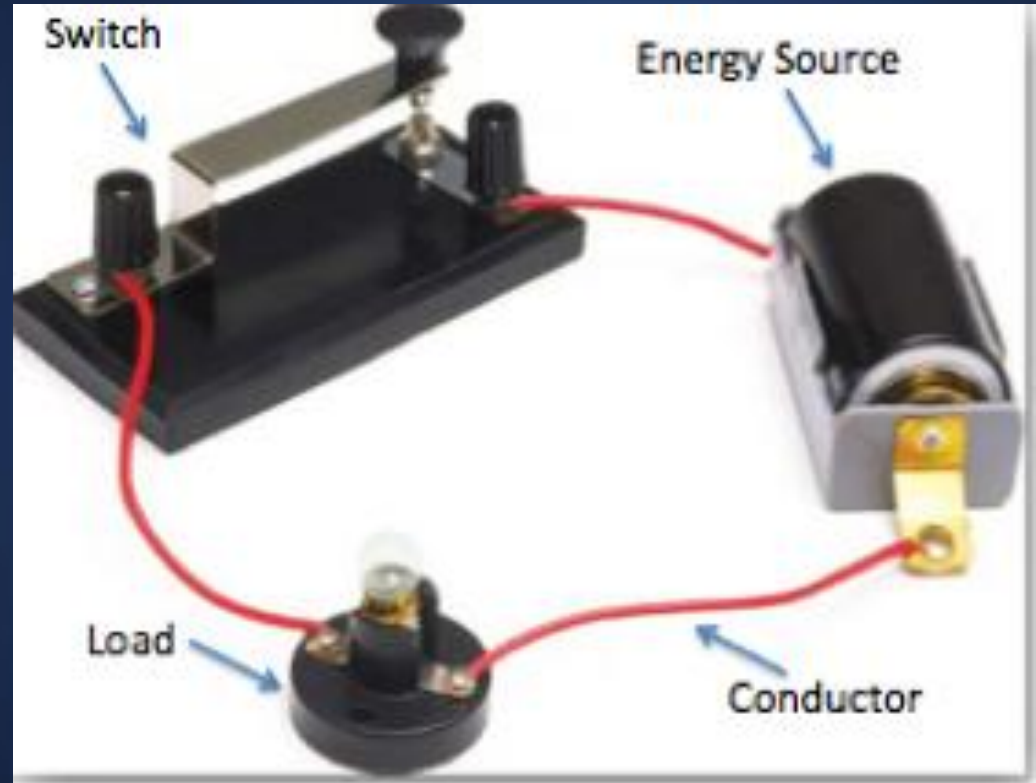- Energy source
- Conductor
- Load
- \* Switch




**Electrons flow from negative to positive**

# Functions of the Parts of a Circuit
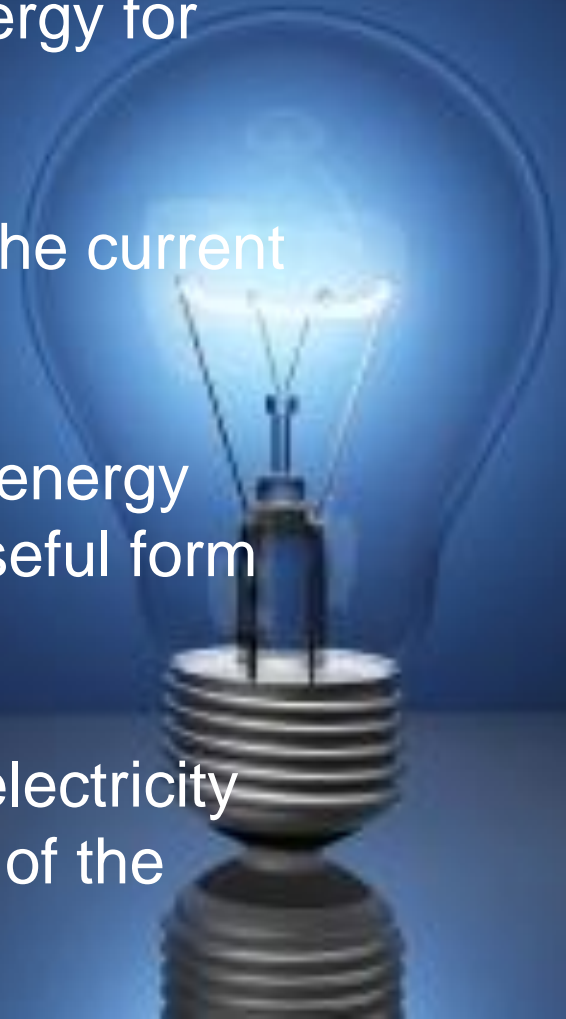
## Parts of a Circuit:

- **Energy source** – provides energy for the electrons in the circuit
- **Conductor** – wires that carry the current (electrons) around the circuit
- **Load** – converts the electrical energy carried by the electrons to a useful form (light, heat, movement)
- \* **Switch** – controls when the electricity can flow (not a necessary part of the circuit)



# Electrochemical Cells

**Electrochemical Cell** = a pack of chemicals that converts chemical energy into electrical energy that is stored in charged particles

- A battery is a combination of electrochemical cells



## Electrochemical cells include:

- **1 Electrolyte**
  - Liquid or paste that conducts electricity
  - Contains chemicals that form ions
  - Ex. Citric acid
- **2 Electrodes**
  - Metal strips that react with the electrolyte
  - Ex. Zinc and Copper

Reaction → electrons collect on one of the electrodes (- charge), and electrons are lost from the other electrode (+ charge)



# Types of Electrochemical Cells

1. Wet
2. Dry
3. Fuel



# Wet Cells

= an electrochemical cell that has a **liquid** electrolyte

Example: Car battery






# Dry Cells

= an electrochemical cell that has a **paste** electrolyte

Example: Simple batteries

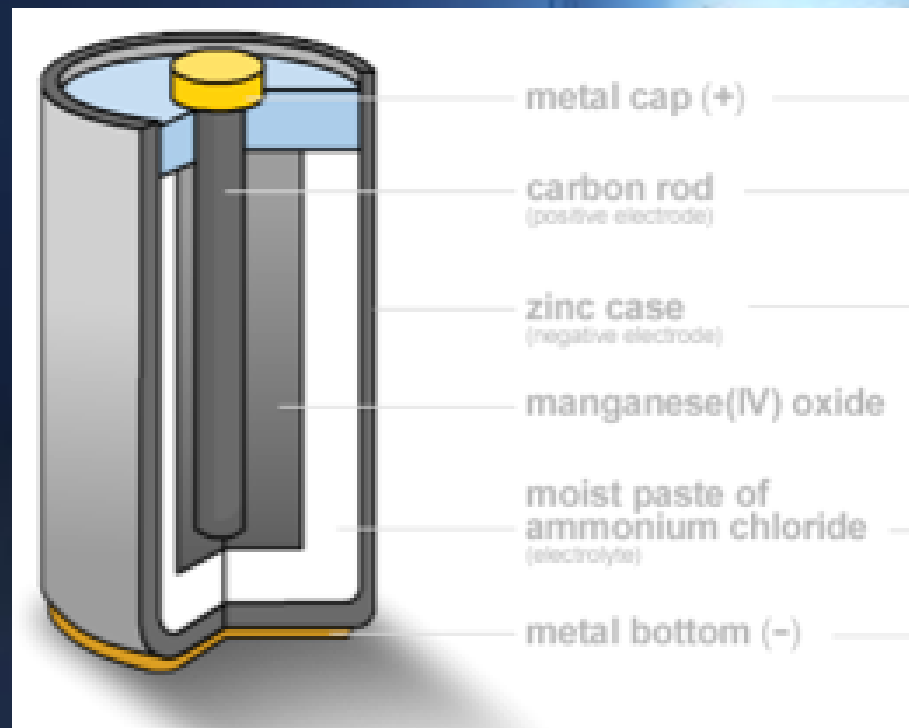

# Fuel Cells

= an electrochemical cell that generates electricity directly from a chemical reaction with fuel

Example: Electric Car Battery



# Homework

A. Questions 1-5 pg. 436

B. Handouts

- The Wet Cell
- How a Dry Cell Battery Works



# Potential Difference, Current and Resistance


- Voltage
- Current
- Resistance
- How to Measure Voltage, Current and Resistance



# Potential Energy

**Potential Energy** = the energy stored in an object


- Every electron has potential energy

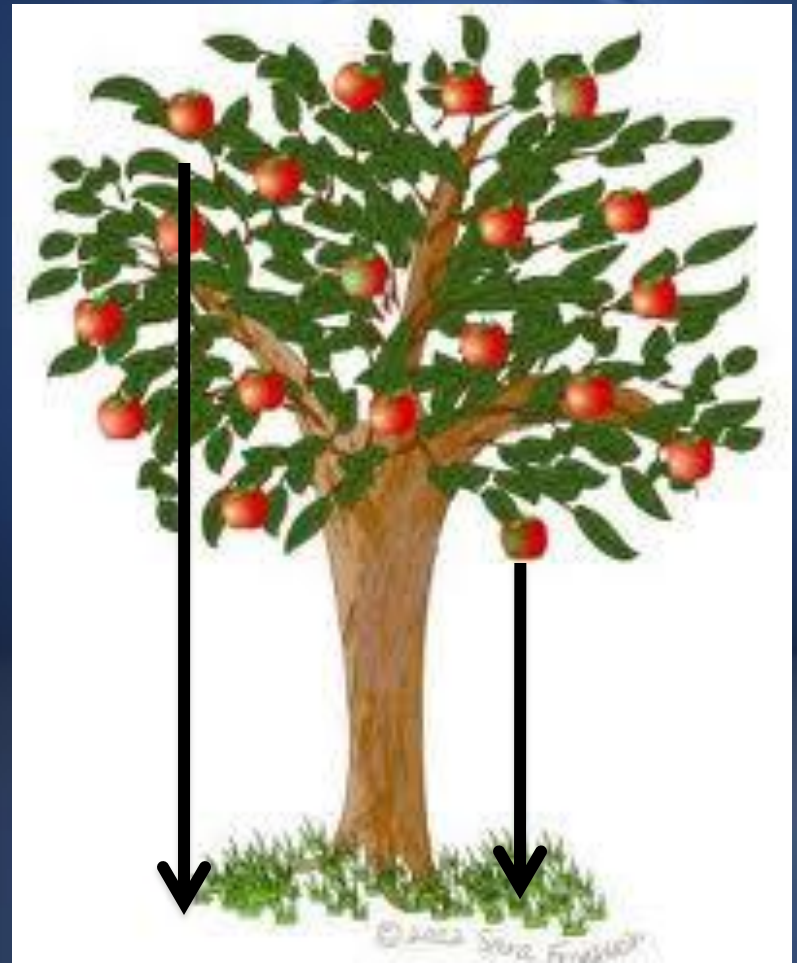
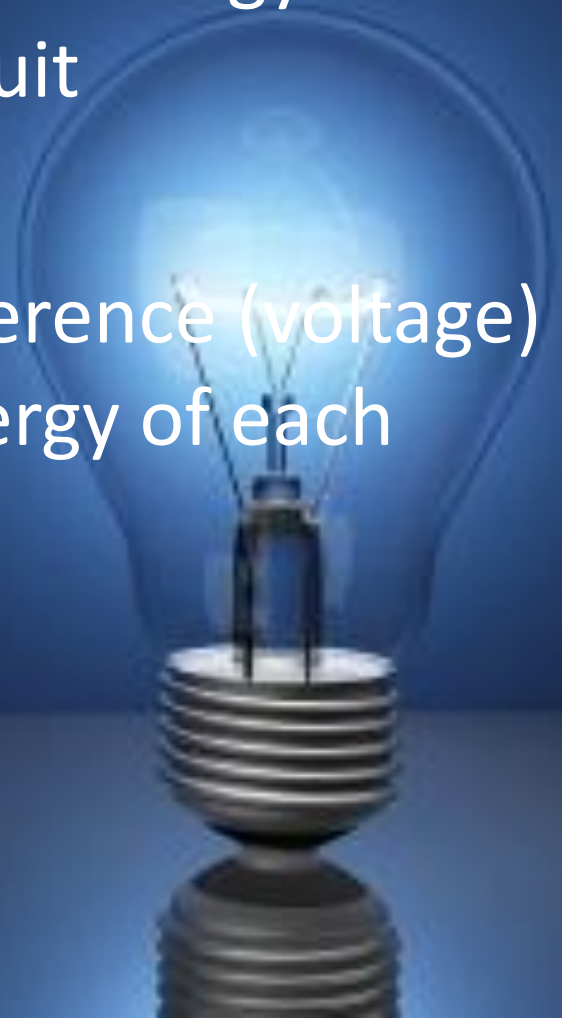
# Potential Difference

**Potential Difference or Voltage (V)** = the difference in electric potential energy between two points in a circuit

- The higher the potential difference (voltage) the greater the potential energy of each electron



# Measuring Potential Difference

**Volt (V)** – is the unit used to measure potential difference


Voltmeter

- Measures the potential difference between two locations in a circuit


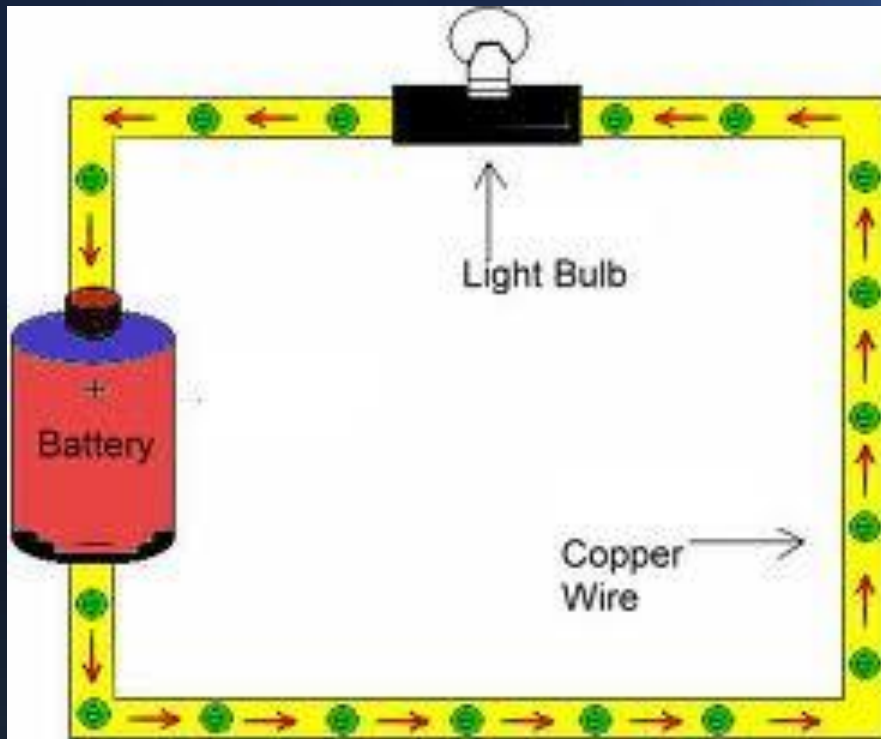
# Electrical Current

**Electrical Current** = is a measure of the amount of electrical charge that passes by a point in an electrical circuit each second






# Types of Current

**Direct Current (DC)** – current that flows in one direction

- Example: current from a battery

**Alternating Current (AC)** – current that flows back and forth in cycles

- Example: current from wall sockets

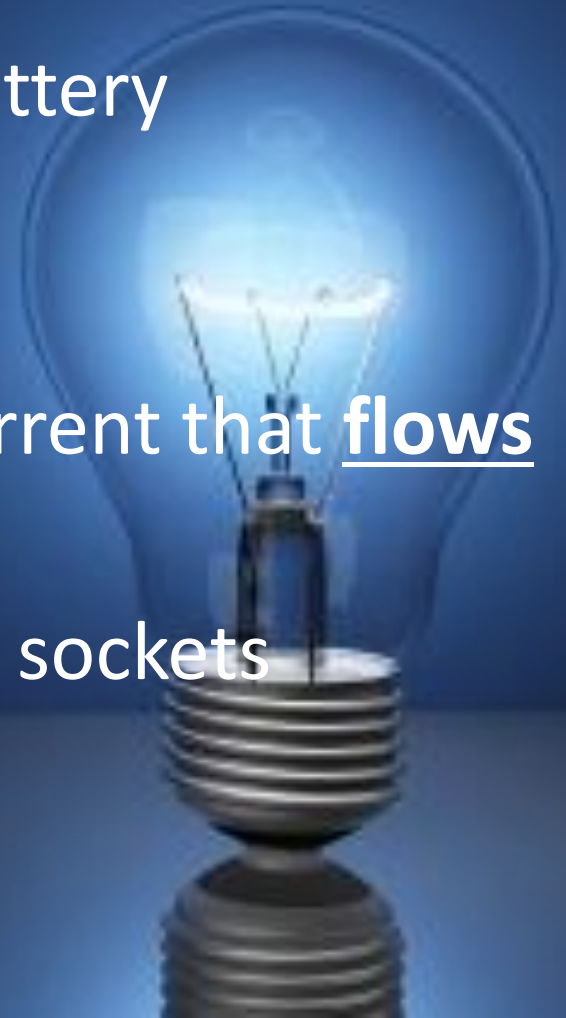

# Measuring Current

**Ampere (A)** – the unit used to measure electric current

Ammeter

- Measures current in a circuit




# Resistance

**Resistance** = the degree of which a substance opposes the flow of electric current through it

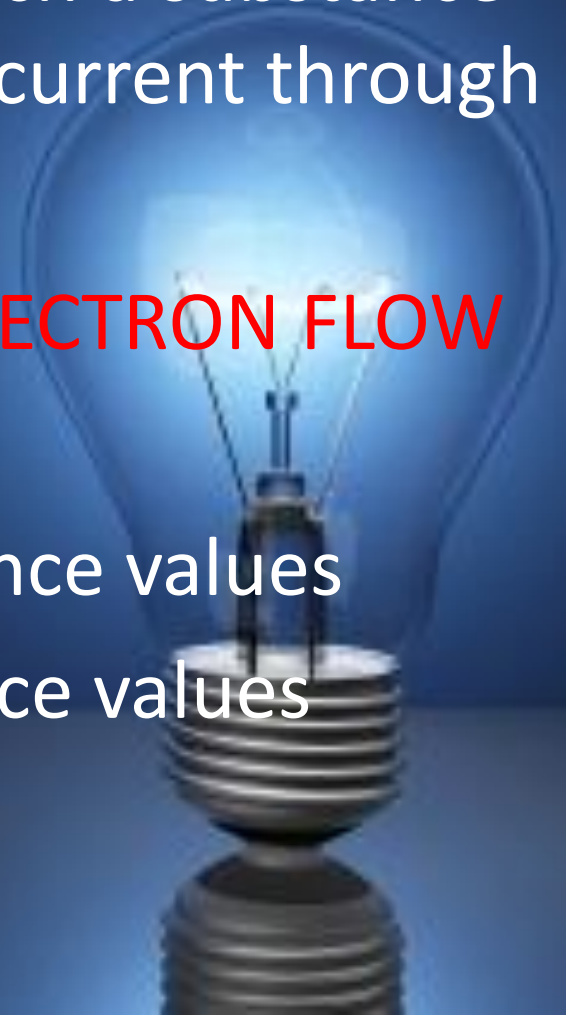**ALL SUBSTANCES RESIST ELECTRON FLOW**

- Conductors have low resistance values
- Insulators have high resistance values



# Example of Resistance

- Light Bulb Filament



# Resistors

- Resistors can be used to control **current** or **potential difference** in a circuit
- The amount of resistance in a circuit affects the electrical current
  - Current decreases if you add resistance



# Factors Affecting Resistance

Table 11.1: Page. 443

Factor	How Factor Affects Resistance
<b>Material</b>	<ul style="list-style-type: none"><li>• The material used in a circuit effects the resistance on the circuit</li><li>• Copper is used most frequently as conducting wire</li></ul>
<b>Temperature</b>	<ul style="list-style-type: none"><li>• High temperatures have a higher resistance</li><li>• Low temperatures have a lower resistance</li></ul>
<b>Length</b>	<ul style="list-style-type: none"><li>• Longer wires have more resistance</li><li>• Shorter wires have less resistance</li></ul>
<b>Cross-sectional Area</b>	<ul style="list-style-type: none"><li>• Wide wires have less resistance</li><li>• Short wires have more resistance</li></ul>

# Measuring Resistance

Ohm ( $\Omega$ ) – the unit used to measure resistance

Ohmmeter

- Measures electrical resistance



# Homework

- A. Questions 3-5 pg. 438
- B. Questions 1-3 pg. 442
- C. Questions 3,4,5,7,8,10 pg.447





# Ohm's Law

$$V = IR$$



# Georg Ohm

- Helped us discover the relationship between voltage, current and resistance

- **Ohm's Law** states:

As long as temperature remains the same,  **$V=IR$**

- $V$  = potential difference
- $I$  = current
- $R$  = resistance



# Ohm's Law



# Steps for Solving Ohm's Law

1. State the information given in the equation and what is required

2. Calculate the solution

**SHOW ALL YOUR WORK !!!!**

3. Write a therefore statement



# Example Problem 1

A current of 4.0 A flows through a 40- $\Omega$  resistor in a circuit. What is the Voltage in the circuit?

(1) GIVEN

$$I \text{ (current)} = 4.0 \text{ A}$$

$$R \text{ (resistance)} = 40 \ \Omega$$

(2) SOLUTION

$$V = I R$$

$$= (4.0 \text{ A}) (40 \ \Omega)$$

$$= 160 \text{ V}$$

(3) Therefore the voltage in the circuit is 160 V.

REQUIRED  
Voltage?

A glowing lightbulb is positioned on the right side of the slide. The bulb is illuminated from within, casting a warm glow. The background is a dark, gradient blue. The text 'REQUIRED Voltage?' is overlaid on the upper right portion of the lightbulb.

# Example Problem 2

A off road jeep has a searchlight with a resistance of  $60 \Omega$  that is placed across a 24-V battery. What is the current in this circuit?

$$R = 60 \Omega$$

$$V = I R$$

$$V = 24 \text{ V}$$

$$I = \frac{V}{R}$$

$$I = ?$$

$$R$$

$$= \frac{24 \text{ V}}{60 \Omega}$$

$$= 0.4 \text{ A}$$

$$= 0.4 \text{ A}$$



Therefore the current in the jeep searchlight is 0.4 A

# Try this one yourself!

A current of 35 A is flowing through a light bulb that is connected to a 124 V power supply. What is the bulb's resistance?

$$I = 35 \text{ A}$$

$$V = I R$$

$$V = 124 \text{ V}$$

$$R = \frac{V}{I}$$

$$R = ?$$

$$\begin{aligned} &= \frac{124 \text{ V}}{35 \text{ A}} \\ &= 3.5 \Omega \end{aligned}$$

Therefore the resistance in the light bulb is 3.5  $\Omega$ .



# Homework

A. All 9 Practice Problems pg 460-461

B. Review Question 1-11 & 13 pg. 447

C. Study for QUIZ

Tomorrow

- Quiz
- Drawing Circuit Diagrams





# Drawing Circuit Diagrams

**Circuit Diagram** – a drawing that uses symbols to show the components and connections in a circuit.


Help to determine how:

- current flows
- device functions







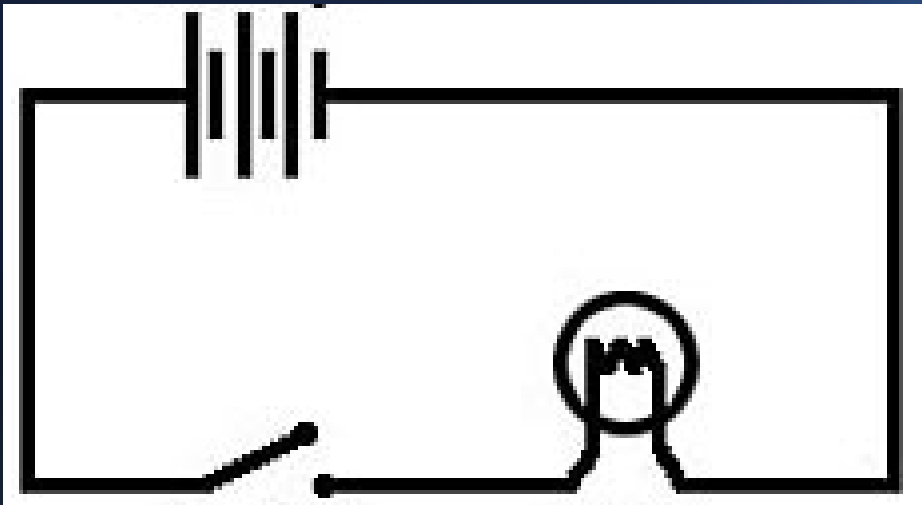


# Rules for Drawing Circuit Diagrams

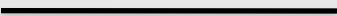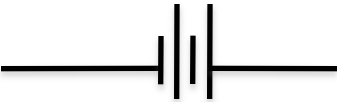1. Always use a ruler
1. Make right-angle corners




# Circuit Diagram Symbols

Table 11.2, pg. 450


Symbol	Component	Function
	Wire	- Conductor; allows electrons to flow
	Cell or Battery	- Electrical source; longer side is positive terminal, shorter side is negative
	Lamp (light bulb)	- Specific load; converts electricity into light and heat
	Resistor	- General load; converts electricity to heat
	Switch	- Opens and closes the circuit
	Ammeter	- Measures current through a device, connected in series
	Voltmeter	- Measures voltage across a device, connected in parallel

# Ohm's Law Review Questions

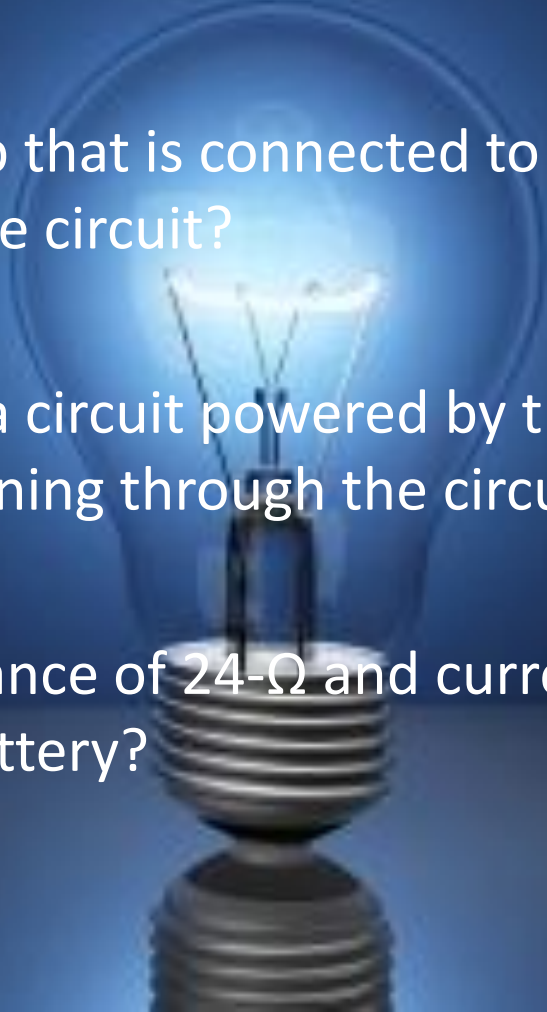1. The current in a circuit is 0.5-A. The circuit has two batteries each with a power supply of 1.3-V. What is the resistance in the circuit?
  1. A current of 400mA runs through a bulb that is connected to two 15- $\Omega$  resistors. What is the voltage in the circuit?
  1. A light bulb has a resistance of 10- $\Omega$  in a circuit powered by three 0.5-V batteries. What is the current running through the circuit?
  1. A circuit with two batteries has a resistance of 24- $\Omega$  and current of 0.5-A. What is the voltage of each battery?
- 
- A glowing light bulb is positioned on the right side of the slide, partially overlapping the text. The bulb is illuminated, with a bright yellow-white light emanating from its filament, and a soft blue glow around it. The base of the bulb is visible, showing the screw threads. The background is a dark blue gradient.
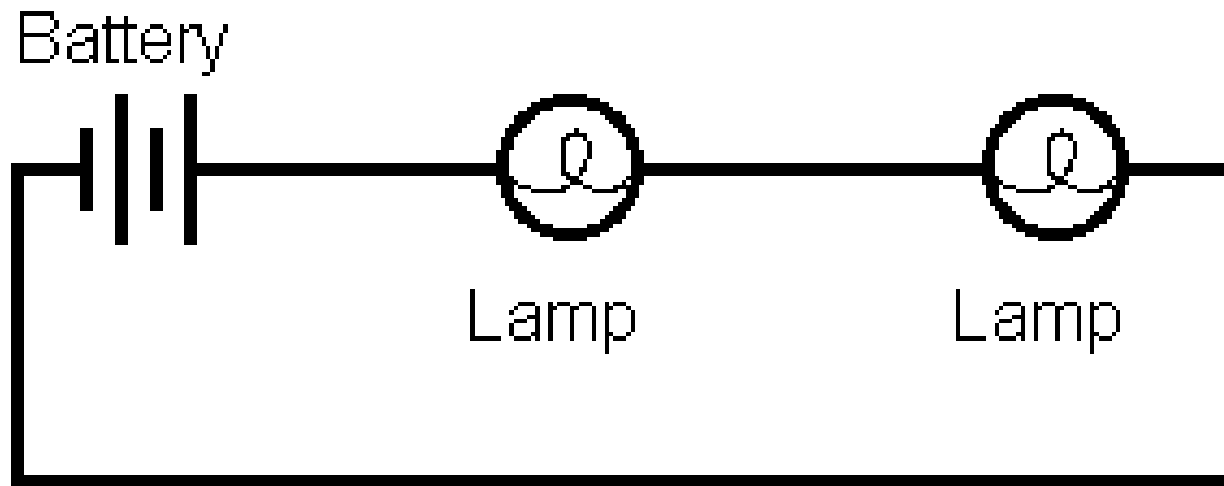
# Series Circuits

**Series Circuit** – an electrical circuit where the components are arranged one after another in a series.




# Series Circuits

- Only has one path where electrons can flow
- If a pathway is interrupted, the whole series is effected
- Current remains the same
- If more resisters are added, resistance increases
- Adding more loads decrease intensity


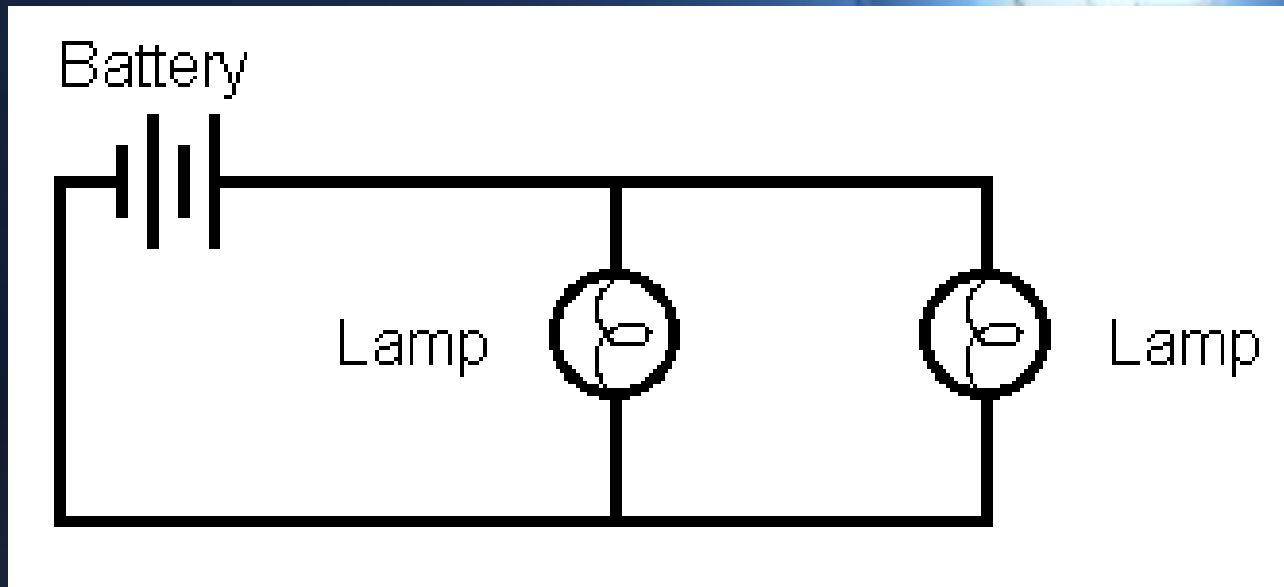
# Parallel Circuits

**Parallel Circuit** – an electrical circuit where the parts are arranged so that electrons can flow along more than one path



# Parallel Circuits

- The point where a circuit divides into different paths is called a junction point
- A break in one pathway does not effect the others
- Adding a new pathway with resistance decrease the total resistance in the circuit
- Most electrons will follow the path with the least resistance; the current on this path is greater

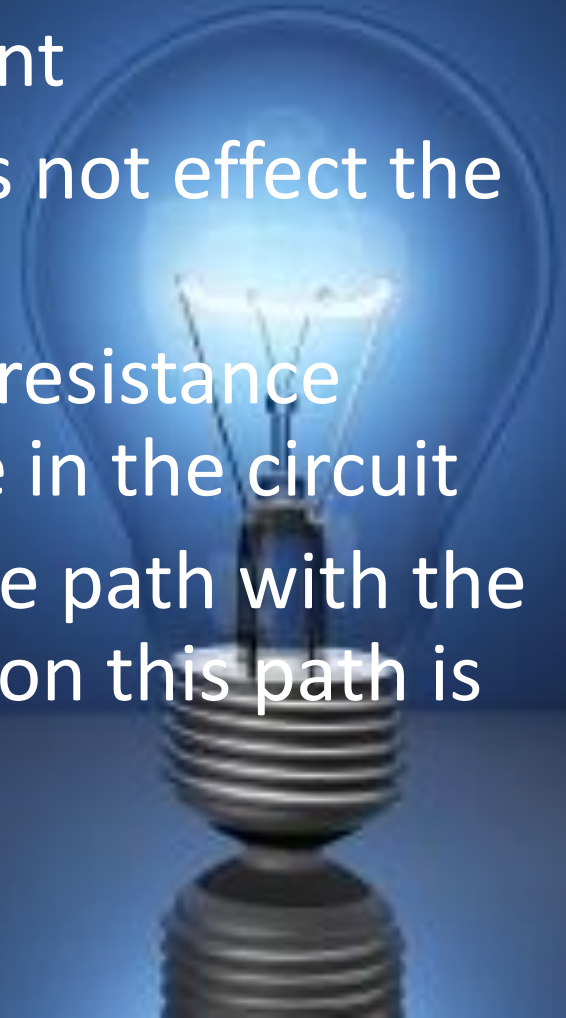




Table 11.3 Potential Difference, Current, and Resistance in Series and Parallel Circuits

Circuit	Potential Difference	Current	Resistance
Series Circuit	Each load uses a portion of the total potential difference supplied by the battery.	The current is the same throughout a series circuit.	The current decreases with more resistors are added.
Parallel Circuit	Each load uses the potential difference supplied by the battery.	The current divides into different paths. A pathway with less resistance will have greater current.	Adding resistors in parallel decreases the total resistance of the circuit.



# Homework

A. Questions 1-5 pg.453

B. Copy Table 11.3 on pg.452 into your notes

Tomorrow

Lab: Series and Parallel Circuits



# Short Circuits and Electrical Safety




# Short Circuits

**Short Circuit** – an accidental low-resistance connection between two points on a circuit, causing excess electron flow

- Can be dangerous

Example:

- Knocked down telephone line

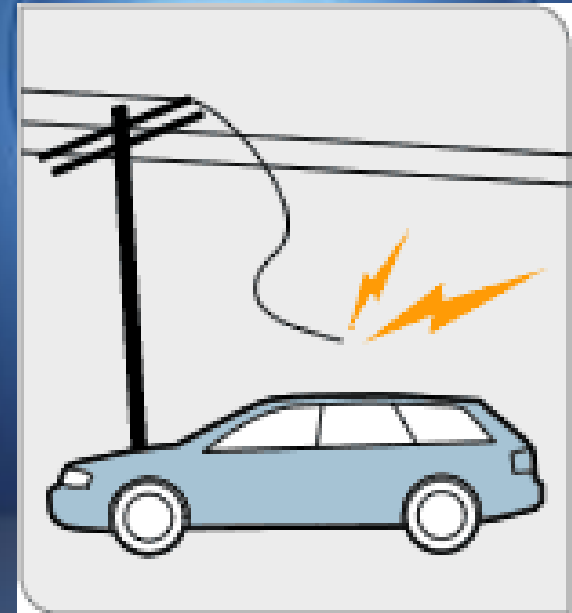

# Electrical Safety

- All electrical appliances present risk
- Some devices retain a charge even when they are unplugged



# Three Prong Plug

- The third prong connects the device to the ground wire of the building
- In case of a short circuit



# Fuses and Circuit Breakers

**Fuse** – a safety device in a electrical circuit that has a metallic conductor with a low melting point compared to the circuit wires



# Circuit Breakers

**Circuit Breaker** – does the same job as a fuse except the wire inside does not melt; it heats up and bends to trigger a spring mechanism





# Ground Fault Circuit Interrupter (GFCI)

- A device that detects change in current and opens the current; stopping flow



# Homework

- Create an poster, song, or website to help promote electrical safety awareness to an elementary school class. Choose information that is relevant and engaging to your audience.

**DUE: TUESDAY, APRIL. 26**

- Lab Report: Due Tomorrow

